

# NEC Microcomputers, Inc.

## Application Note 14

### Power-On-Reset Circuitry For $\mu$ Com-4 Microcomputer Designs

Any product designed around one of the  $\mu$ COM-4 4-bit single chip microcomputers will require connection of some external circuitry to the RESET input for correct operation. This circuitry ensures the proper timing sequence for the various portions of the microcomputer's internal logic during power-up. The product design engineer should be aware of several approaches to this circuitry design and the associated cost-performance trade-offs.

Under ideal conditions, the rise time ( $t_r$ ) of the RESET input signal need not be very fast. Once the high level is reached, the RESET input signal should remain stable at that level for a minimum of 4 instruction cycles (40  $\mu$ s). The fall time ( $t_f$ ) of the RESET input signal should be as short as possible to minimize any possible effects of noise. The  $t_f$  should be less than one instruction cycle (10  $\mu$ s) for optimal performance.


Under actual conditions, the design engineer should make  $t_f$  as close to 10  $\mu$ s as possible while maintaining the overall cost-performance objectives for his product. The application engineers at NEC Microcomputers, Inc. have developed several implementations of the external power-on-reset circuitry which

allow the design engineer to attain those objectives. All of these circuits work equally well with the following  $\mu$ COM-4 4-bit microcomputers:


$\mu$ PD546	$\mu$ PD547	$\mu$ PD550
$\mu$ PD553	$\mu$ PD547L	$\mu$ PD550L
$\mu$ PD556	$\mu$ PD552	$\mu$ PD554
$\mu$ PD557L	$\mu$ PD651	$\mu$ PD554L
$\mu$ PD650		$\mu$ PD652

For products where there is little or no noise on the power supply lines, as with a battery power supply design, the  $t_f$  requirements of the RESET input signal are not critical. The design engineer can obtain very satisfactory system performance at low cost with the power-on-reset circuit shown in Figure 1.


For products where there is noise on the power supply lines, as with switching or A/C-transformer power supply designs, the  $t_f$  requirements of the RESET input signal are critical, and the above circuit does not provide a fast enough  $t_f$  for consistently good performance. Instead, the design engineer can obtain very satisfactory system performance at reasonable cost with either of the power-on-reset circuits shown in Figure 2.

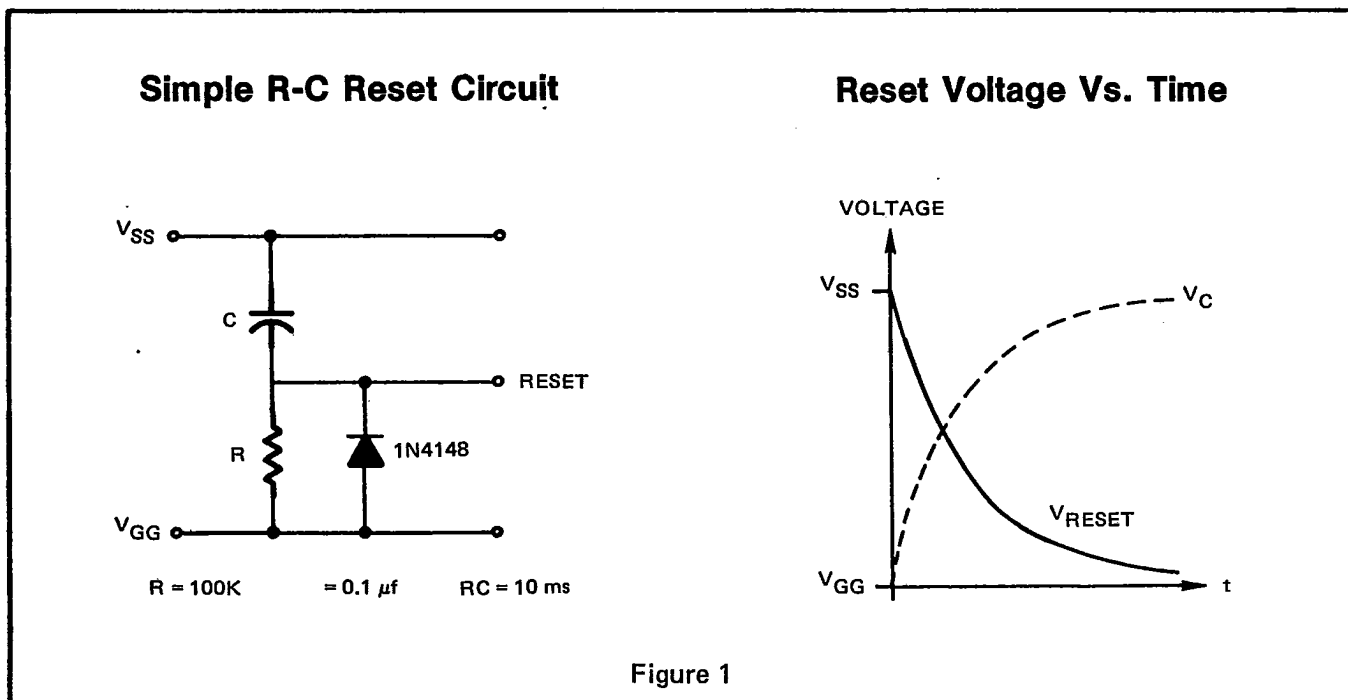


### Transistor-Switch Reset Circuit

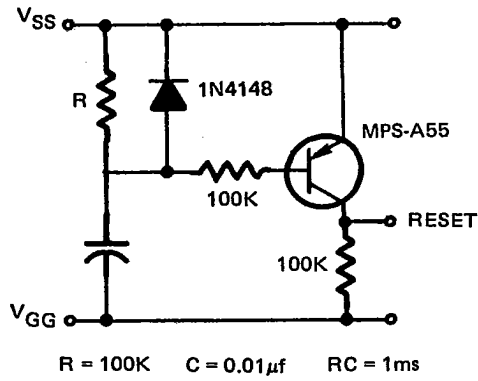

### Reset Voltage Vs. Time

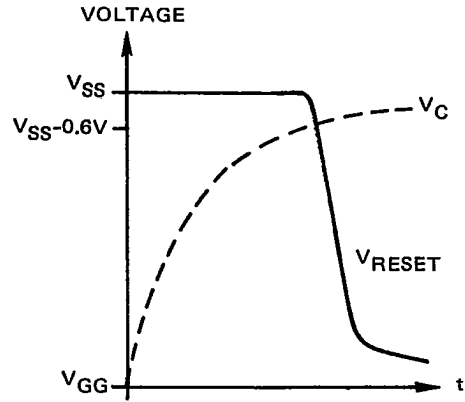

### Comparator Reset Circuit

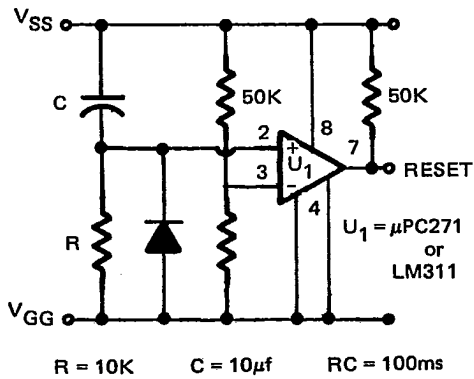

### Reset Voltage Vs. Time

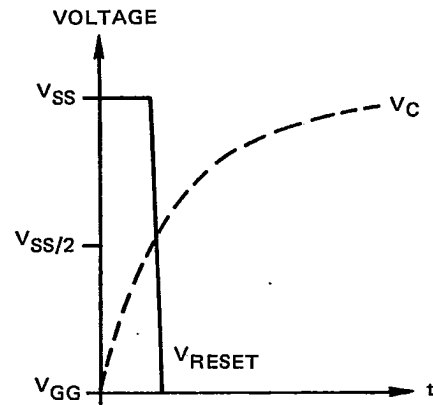


Figure 2

**NEC Microcomputers, Inc.**

173 Worcester Street/Wellesley, Massachusetts 02181  
 Telephone 617/237-1910 TWX 710-383-1745

The information presented in this document is believed to be accurate and reliable. It is subject to change without notice.

©1981 NEC Microcomputers, Inc.  
 PRINTED IN U.S.A.

AN14-2-81-8K