

AY-3-1350 continuous reading

The Elektor board (november 1980) used the automatic stopping function to stop the AY-3-1350 after each melody playing.

It is really simple to power the board in order to use the board all the time to read :

- the melodies one after the other
- a melody in particular
- all the 25 melodies

Modification

Suppress

- D1 to D17,
- R10 and R12,
- C3, C4, C5 and C8,

Replace:

- T1 with a 78L05 (connect the GND of the regulator)
- R9 and D18 with a 100nF capacitor
- R11 by a strap,

on the AY-3-1350,

- leave pin 15 not connected
- connect pin 9 to the common ES1-ES4 by connecting **P** and **N**,
- connect **R** to pin 17 ("restart" function),
- connect **S** to pin 10 ("next tune" function).

Use

$S_A \rightarrow$ read one melody (chosen by connecting **A**, **B**, **C**, **D**, or **E** to GND or pin 15 to **K**, **L**, **M**, or **N**) in loop if connected.

$S_B \rightarrow$ read each melody one after the other or in loop in maintained.


$S_G \rightarrow$ reading one octave lower.

improvements...

New melodies by using 9 ports (D0-D7 +A0) of a Arduino card to simulate a external eprom.

Use another chip as the AY-3-8910/30...

modified schematic

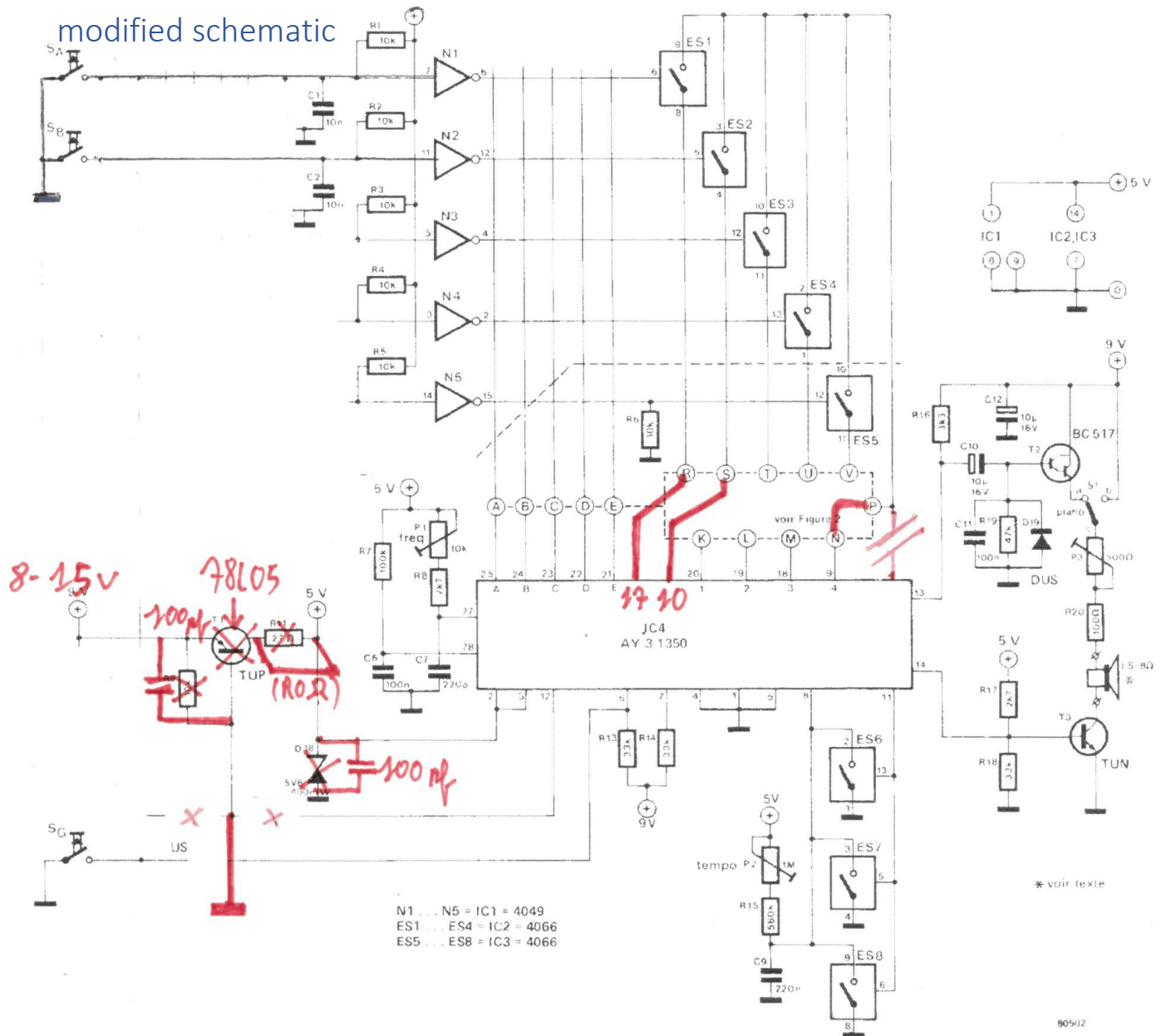

PCB

